

SMART DEVICES

Non-linear Resistive Sensors

Josué ALVAREZ, Cyril ANAK STELL, Aminata DIOP,
Cécile DUTHOIT, Linn MJELSTAD, Clovis OUEDRAOGO

December 2016

1 Introduction

This document answers an exercise about resistive sensors and how to choose the appropriate electrical assembly to power this sensor. It discusses non-linearity reduction of the measurement on non-linear resistive sensors, such as the one we made during our AIME internship. Five different types of potentiometric assemblies will be discussed and compared:

- Potentiometric assembly powered by a voltage or current source
- Quarter-bridge arm
- Half bridge
- Push-pull
- Active quarter-bridge arm linearization

2 Resistive Sensor

2.1 Question 5.1 - Deviation from linearity

The deviation from linearity is the most important deviation within the measurements between the real feature and its linear approximation. The extreme values pour m are here 0 and 2, which leads to R_c :

$$\delta R_c = \max(R_c - R_{c,lin}), m \in [0; 2]$$
$$\delta R_c = 0,19 \quad \Omega$$

2.2 Question 5.2 - Linearity error

The linearity error is the deviation from linearity divided by the difference between both extreme values of the sensor output, which is here its resistance:

$$\epsilon = \frac{\delta R_c}{\max(R_c) - \min(R_c)} = \frac{0,19}{121,20 - 100} = 0,9 \quad \%$$

2.3 Question 5.3 - Sensor sensibility

Using the linear approximation given at the beginning of the exercise, we got S_c , the sensor sensibility:

$$S_c = \frac{\Delta R_c}{\Delta m} = b' = 10,6 \quad \Omega/m's \quad unity$$

2.4 Question 5.4

It is better to choose a value at the middle of all the measurement values already done, in order to limit the non-linearity and the uncertainties. We can choose 1 here. By reading the table of results for $m_0 = 1$, we get:

$$R_c(m_0) = R_{c0} = 110,30 \quad \Omega$$

2.5 Question 5.5

We want to demonstrate that $\Delta R_c = A\Delta m^2 + B\Delta m$

$$\begin{aligned}\Delta R_c &= R_c(m) - R_{c0} \\ \Delta R_c &= R_c(m_0 + \Delta m) - R_{c0} \\ \Delta R_c &= a(m_0 + \Delta m)^2 + b(m_0 + \Delta m) + c - (am_0^2 + bm_0 + c) \\ \Delta R_c &= a\Delta m^2 + (b + 2am_0)\Delta m \\ \Delta R_c &= A\Delta m^2 + B\Delta m\end{aligned}$$

We get the expression we were looking for.

3 Potentiometer installation - Current supply

3.1 Question 5.6

Voltage divider:

$$V_{mes} = \frac{R_c}{R + R_c} V_g = \frac{R_{c,0} + \Delta R_c}{R + R_{c,0} + \Delta R_c} V_g \quad (1)$$

3.2 Question 5.7

$$V_{mes} = \Delta V_{mes} + V_{mes,0} \Rightarrow \Delta V_{mes} = V_{mes} - V_{mes,0} \quad (2)$$

$$\begin{aligned}\Delta V_{mes} &= \frac{R_{c,0} + \Delta R_c}{R + R_{c,0} + \Delta R_c} V_g - \frac{R_{c,0}}{R + R_{c,0}} V_g \\ &= \frac{(R_{c,0} + \Delta R_c)(R + R_{c,0})}{(R + R_{c,0} + \Delta R_c)(R + R_{c,0})} V_g - \frac{R_{c,0}(R + R_{c,0} + \Delta R_c)}{(R + R_{c,0})(R + R_{c,0} + \Delta R_c)} V_g \\ &= \frac{R_{c,0}R + R_{c,0}R_{c,0} + \Delta R_c R + \Delta R_c R_{c,0} - RR_{c,0} - R_{c,0}R_{c,0} - R_{c,0}\Delta R_c}{RR + RR_{c,0} + R\Delta R_c + RR_{c,0} + R_{c,0}R_{c,0} + R_{c,0}\Delta R_c} V_g \\ &= \frac{\Delta R_c R}{RR + 2RR_{c,0} + R_{c,0}R_{c,0} + \Delta R_c(R + R_{c,0})} V_g \\ &= \frac{\Delta R_c R}{(R + R_{c,0})^2 + \Delta R_c(R + R_{c,0})} V_g\end{aligned} \quad (3)$$

3.3 Question 5.8

We are looking for the value of R that gives us $\frac{d\Delta V_{mes}}{dR} = 0$.

Derived the expression becomes :

$$\frac{d\Delta V_{mes}}{dR} = \frac{R_c - R_{c,0}}{(R_{c,0} + R)^2(R_c + R)^2} V_g (R_c R_{c,0} - R^2) = 0 \quad (4)$$

R_c is evolving around $R_{c,0}$ and therefore we chose to use $R = R_{c,0}$. Which gives us:

$$\Delta V_{mes} = \frac{\Delta R_c}{4R_{c,0}(1 + \frac{\Delta R_c}{2R_{c,0}})} V_g = \frac{A\Delta m^2 + B\Delta m}{4R_{c,0}(1 + \frac{A\Delta m^2 + B\Delta m}{2R_{c,0}})} V_g \quad (5)$$

4 Montage potentiométrique - Alimentation en courant

4.1 Question 5.12

Expression of $V_{mes} = f(R_c \text{ and } I_g)$:

$$V_{mes} = R_c I_g \quad (6)$$

Let's calculate the variation ΔV_{mes} with Δm and ΔR_c evolution:

$$\begin{aligned}\Delta V_{mes} &= V_{mes} - V_{mes,0} \\ &= R_c I_g - R_{c,0} I_g \\ &= I_g \Delta R_c\end{aligned}\tag{7}$$

Where :

$$\begin{aligned}\Delta R_c &= R_c - R_{c,0} \\ &= a\Delta(m^2) + b\Delta m\end{aligned}\tag{8}$$

4.2 Question 5.13

Expression of $\Delta V_{mes,lin}$, the linear approximation of ΔV_{mes} :

$$\begin{aligned}\Delta V_{mes,lin} &= I_g \Delta R_{c,lin} \\ &= I_g (R_c - R_{c,0}) \\ R_{c,lin} = b'm - c' &= I_g (bm + c' - b'm_0 - c') \\ &= I_g b' (m - m_0) = I_g b' \Delta m\end{aligned}$$

4.3 Question 5.14

Comparaison with "Alimentation en tension":

4.4 Question 5.15

Expression of error of linearity ϵ_2 :

$$\epsilon_2 = \Delta V_{mes} - \frac{\Delta V_{mes,lin}}{\Delta V_{mes}}\tag{10}$$

If

$$\Delta V_{mes} \simeq \Delta V_{mes,lin}\tag{11}$$

thus

$$\epsilon_2 = \Delta V_{mes,lin} - 1\tag{12}$$

4.5 Question 5.16

The expression of V_{mes} :

$$V_{mes} = \left(\frac{R_c}{R_c + R_1} + \frac{R_3}{R_3 + R_2} \right) V_g = \frac{R_c R_2 - R_1 R_3}{(R_c + R_1)(R_3 + R_2)} V_g$$

4.6 Question 5.17

Balancing the bridge for the value m_0 of the measurand is equivalent to $R_{c0} R_2 - R_1 R_3 = 0$.

$$V_{mes} = \frac{R_c R_2 - R_1 R_3}{(R_c + R_1)(R_3 + R_2)} V_g = 0 \Rightarrow R_c R_2 - R_1 R_3 = 0$$

It is necessary to choose $R_1 = R_{c0}$ to have a better sensitivity in the potentiometric branch containing the sensor. This results is $R_2 = R_3$. In order to have the same power dissipated by the joule effect on each of the resistors (including the sensor) so as to balance the heating, $R_1 = R_2 = R_3 = R_{c0} = 110.30\Omega$. So the expression of V_{mes} become:

$$V_{mes} = \frac{R_c - R_{c0}}{R_c + R_{c0}} \frac{V_g}{2}$$

4.7 Question 5.18

The measurement voltage is written as:

$$V_{mes} = \Delta V_{mes} = \frac{\Delta R_c}{2R_{c0}(1 + \frac{\Delta R_c}{2R_{c0}})} \frac{V_g}{2} = \frac{B\Delta m(1 + \frac{A}{B}\Delta m)}{1 + \frac{A\Delta m^2 + B\Delta m}{2R_{c0}}} \frac{V_g}{4R_{c0}}$$

4.8 Question 5.19

The linear approximation $\Delta V_{mes,lin}$ of ΔV_{mes} is given by the first order expansion in Δm , that is:

$$\Delta V_{mes,lin} = \frac{BV_g}{4R_{c0}} \Delta m$$

4.9 Question 5.20

The reduced sensitivity x of the measurement is deduced therefrom:

$$S_r = \frac{1}{V_g} \frac{\Delta V_{mes,lin}}{\Delta m} = \frac{B}{4R_{c0}}$$

$$S_r = 24 \text{mV per unit of m/V}$$

4.10 Question 5.21

The linearity error is calculated as in the case of potentiometric power supplied:

$$\epsilon_3 = \frac{(\frac{A}{B} - \frac{B}{2R_{c0}})\Delta m - \frac{A}{2R_{c0}\Delta m^2}}{1 + \frac{A}{B}\Delta m}$$

The expansion to order 2 in Δm of the above expression gives:

$$\epsilon_3 = (\frac{A}{B} - \frac{B}{2R_{c0}})\Delta m - \frac{A^2}{B^2}\Delta m^2 = -1,97.10^{-2}\Delta m - 8,01.10^{-4}\Delta m^2$$

This term is maximum for: $\Delta m = 1$ and $\epsilon_3 = -2,10\%$

5 Montage en demi-pont push-pull

In this part, we consider a second sensor identical to R_c that we substitute to R_1 . R_c and R_1 are in push-pull mode.

5.1 Question 5.22

The balance of the bridge is still realised for the value m_0 .

We have replaced R_1 with a sensor with the same characteristics as R_c . Because it is a push-pull mounting the value of all the four resistance will be the same at the beginning. We also know that $V_{mes,0} = 0$. This means that $R_2 = R_3 = R_{c0}$, we also know that $R_{1,0} = R_{c,0}$. We have $R_c = R_{c0} + \Delta R_c$, and $R_1 = R_{1,0} + \Delta R_1 = R_{c,0} + \Delta R_1$. We also know that $V_{mes,0} = 0$, which means that $V_{mes} = V_{mes,0} + \Delta V_{mes}$ becomes $V_{mes} = \Delta V_{mes}$. V_{mes} will be measured at the same point as earlier, and we therefore got:

$$\Delta V_{mes} = V_{mes} = \frac{R_c}{R_1 + R_c} V_g - \frac{R_3}{R_2 + R_3} V_g = \frac{R_{c,0} + \Delta R_c}{R_{c,0} + \Delta R_1 + R_{c,0} + \Delta R_c} V_g - \frac{R_{c,0}}{R_{c,0} + R_{c,0}} V_g \quad (13)$$

$$\Delta V_{mes} = (\frac{R_{c,0} + \Delta R_c}{R_{c,0} + \Delta R_c + R_{c,0} + \Delta R_1} - \frac{R_{c,0}}{2R_{c,0}}) V_g \quad (14)$$

$$\Delta V_{mes} = \frac{(V_g)(\Delta R_c - \Delta R_1)}{4(R_{c,0} + \Delta R_1)} \quad (15)$$

5.2 Question 5.23

As mentioned earlier, the two sensors R_c and R_1 are identical, and in push-pull mode. So, we got :

$$\Delta R_c = R_c(m_0 + \Delta m) - R_c(m_0) = A\Delta m^2 + B\Delta m \quad (16)$$

$$\Delta R_c = R_c(m_0 - \Delta m) - R_c(m_0) = A\Delta m^2 - B\Delta m \quad (17)$$

5.3 Question 5.24

With the new expressions of ΔR_c and ΔR_1 , ΔV_{mes} can be written as :

$$\Delta V_{mes} = \frac{V_g * B * \Delta m}{2(R_{c0} + A\Delta m^2)}$$

5.4 Question 5.25

In order to achieve the linear approximation, we must first put rewrite ΔV_{mes} :

$$\Delta V_{mes} = \frac{V_g * B * \Delta m}{2R_{c0}(1 + \frac{A\Delta m^2}{R_{c0}})}$$

Because $R_{c0} \gg A \Delta m^2$, we have :

$$\Delta V_{mes,lin} = \frac{V_g * B * \Delta m}{2R_{c0}}$$

5.5 Question 5.26

The reduced sensibility of the measure is given by :

$$\begin{aligned} S_r &= \frac{1}{V_g} \frac{\Delta V_{mes,lin}}{\Delta m} \\ S_r &= \frac{1}{V_g} \frac{B * V_g * \Delta m}{2R_{c0} * \Delta m} \\ S_r &= \frac{B}{2R_{c0}} \end{aligned}$$

6 Linéarisation amont - Montage en quart de pont actif

6.1 Question 5.28

Supposing that the operational amplifier is ideal, we have the following:

$$V_B = \frac{R_{c,0}}{2R_{c,0}} V_g = \frac{V_g}{2} \quad (18)$$

$$V_A = V_{mes} + \frac{R_c}{R_c + R_{c,0}} (V_g - V_{mes}) = \frac{R_c}{R_c + R_{c,0}} V_g + (1 - \frac{R_c}{R_c + R_{c,0}}) V_{mes} = \frac{R_c}{R_c + R_{c,0}} V_g + (\frac{R_c + R_{c,0}}{R_c + R_{c,0}} - \frac{R_c}{R_c + R_{c,0}}) V_{mes} \quad (19)$$

$$V_A = \frac{R_c}{R_c + R_{c,0}} V_g + \frac{R_{c,0}}{R_c + R_{c,0}} V_{mes} \quad (20)$$

6.2 Question 5.29

As the operation amplifier is supposed to be ideal, we have the following relation: $V_A = V_B$ This will give us the following:

$$\frac{V_g}{2} = \frac{R_c}{R_c + R_{c,0}} V_g + \frac{R_{c,0}}{R_c + R_{c,0}} V_{mes} \quad (21)$$

$$(\frac{1}{2} - \frac{R_c}{R_c + R_{c,0}}) V_g = \frac{R_{c,0}}{R_c + R_{c,0}} V_{mes} \quad (22)$$

$$(\frac{R_c + R_{c,0}}{2R_{c,0}} - \frac{R_c}{R_{c,0}}) V_g = V_{mes} \quad (23)$$

$$V_{mes} = \frac{R_{c,0} - R_c}{2R_{c,0}} V_g \quad (24)$$

We know that $\Delta R_c = R_c - R_{c,0}$ and this will give us the following:

$$V_{mes} = \frac{-\Delta R_c V_g}{2R_{c,0}} \quad (25)$$

From the previous equations, we can deduce that:

$$V_{mes} = \Delta V_{mes} = \frac{-BV_g \Delta m}{2R_{c,0}} (1 + \frac{A}{B} \Delta m) \quad (26)$$

6.3 Question 5.30

The linear approximation of $\Delta V_{mes,lin}$ of V_{mes} is:

$$\Delta V_{mes,lin} = \frac{-BV_g \Delta m}{2R_{c,0}} \quad (27)$$

6.4 Question 5.31

We can now deduce the expression of the reduced sensitivity of the measure as the following:

$$S_r = \frac{\Delta V_{mes,lin}}{\Delta m V_g} \quad (28)$$

Then we will have:

$$S_r = \frac{-B}{2R_{c0}} \quad (29)$$

This will help us obtain the numerical value of the reduced sensibility which is -48mV/m/V.

6.5 Question 5.32

The linearity error is calculated like the following:

$$\epsilon_5 = \frac{\frac{-BV_g \Delta m}{2R_{c0}}(1 + \frac{A\Delta m}{B}) + \frac{BV_g \Delta m}{2R_{c0}}}{\frac{-BV_g \Delta m}{2R_{c0}}(1 + \frac{A\Delta m}{B})} = \frac{A\Delta m}{B + A\Delta m} \quad (30)$$

For the second order, we get the following:

$$\epsilon_5 \approx \frac{A\Delta m}{B} \left(1 - \frac{A\Delta m}{B}\right) \quad (31)$$

When $\Delta m = -1$, this expression is at it's maximum and will give us:

$$\epsilon_5 = -2.91\% \quad (32)$$